

## Introduction

The product modeled using the Logisim 2.7.1 tool consists of an 8-bit Pico processor and a 32 x 8 RAM memory. It includes the following components: "Program Counter", "Memory Address Register", "Memory Buffer Register", Instruction Register, the "Accumulator", and the "Arithmetic Logic Unit". Along with these, there are address and data buses, which enable communication between the CPU and the memory. The processor follows a basic set of instructions that include memory read and write operations, logical operations such as negation, arithmetic operations like addition, and system detection. Other instructions in the instruction set include "LOAD", "STORE", "ADD", "INC", "NOT", and "HLT". No conditional jump instructions were made. It operates with 8-bit words, as instructions and data are processed in 8-bit blocks. Communication within the CPU occurs through the two main buses: the "Address Bus" and the "Data Bus". The "Address Bus" carries the memory address, and the Data Bus transfers data between the CPU and the RAM. It is worth noting that the system mimics the Von Neumann architecture, where instructions and data are stored in a single memory that allows the immediate execution of instructions stored sequentially.


# Operation of the System

## Initiation of the system

### LOAD instruction example


Como se muestra en la Figura 1, para iniciar el sistema se requieren realizar los siguientes pasos:

1. **Activate the Enable and CLOCK.**
2. **Press PINS:**
  - i. **MANUAL THICK**
  - ii. **PROGRAM COUNTER**
  - iii. **MEMORY ADDRESS REGISTER**

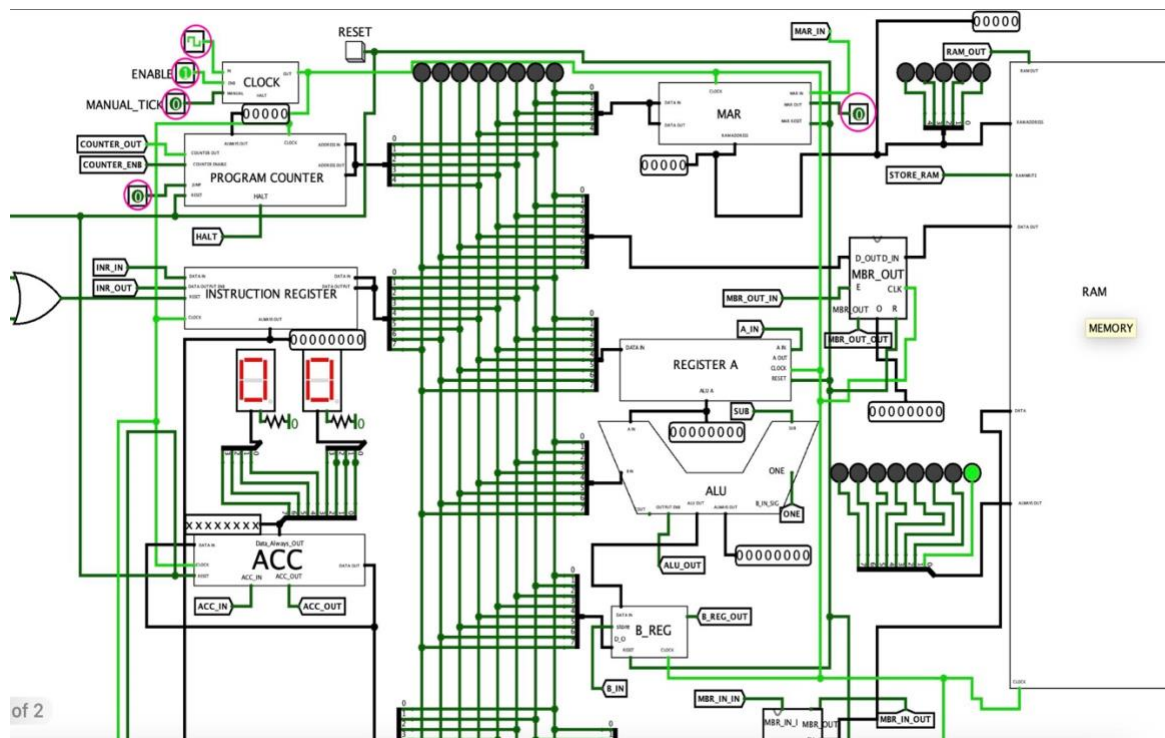


**Figure 1:** Schematics of step #1 and #2 in Logisim.

3. **STORE in RAM:**
  - i. **In ADDRESS 0: The value 01 = (LOAD 00001).**
  - ii. **In ADDRESS 1: The value 03 = (LOAD value 3 in ACC)**

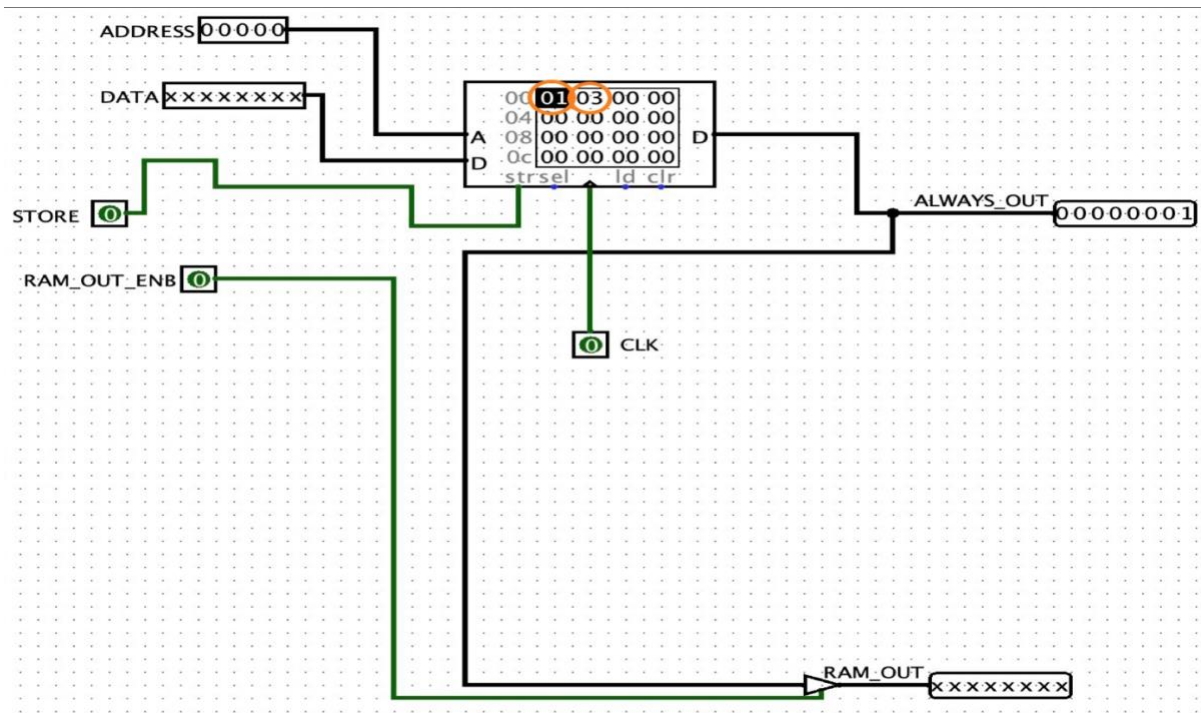

**Figure 2:** Schematics of step #3 in Logisim


4. Simulate the circuit.

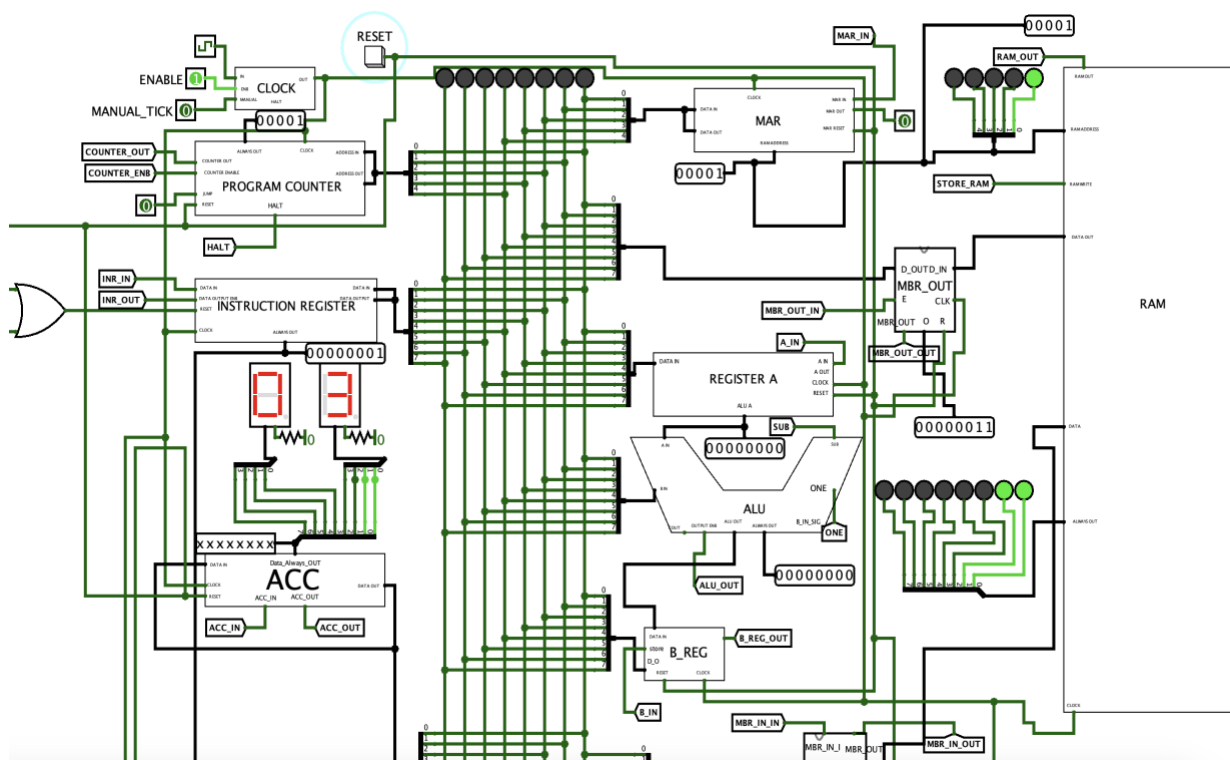


**Figure 3:** Simulation schematics for the CPU.

## Simulation of the System

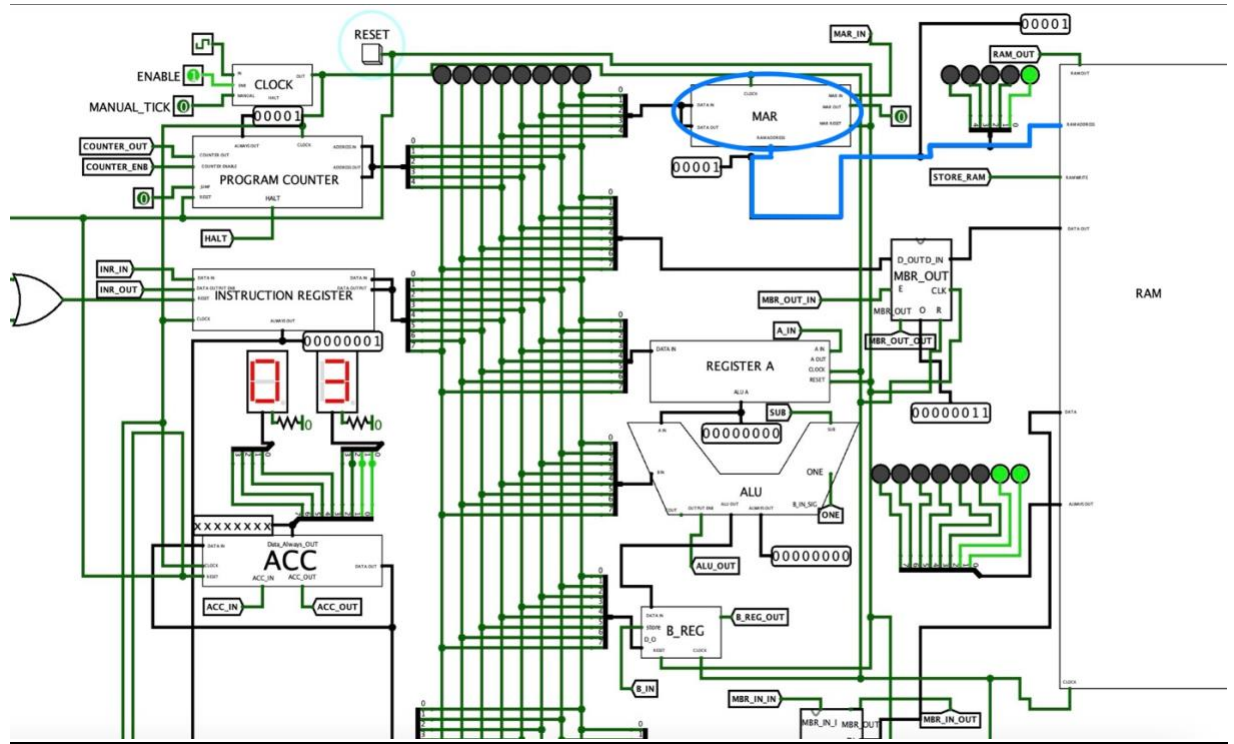
1. In the RAM, the address 0 contains the value 01.
2. On the first CLOCK pulse, the PC sends ADDRESS 0 to the MAR using the control signals COUNTER\_OUT and MAR\_IN.



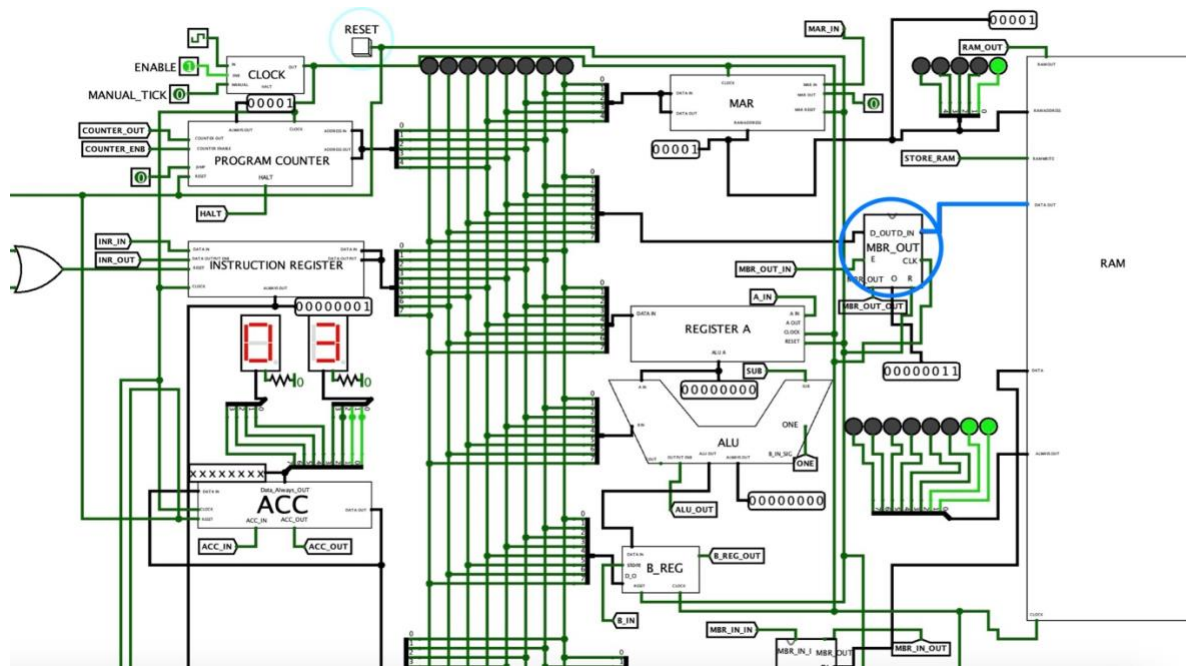
3. In the second CLOCK pulse, the RAM sends the contents of memory location 0 to the MBR using the control signals RAM\_OUT and MBR\_IN.



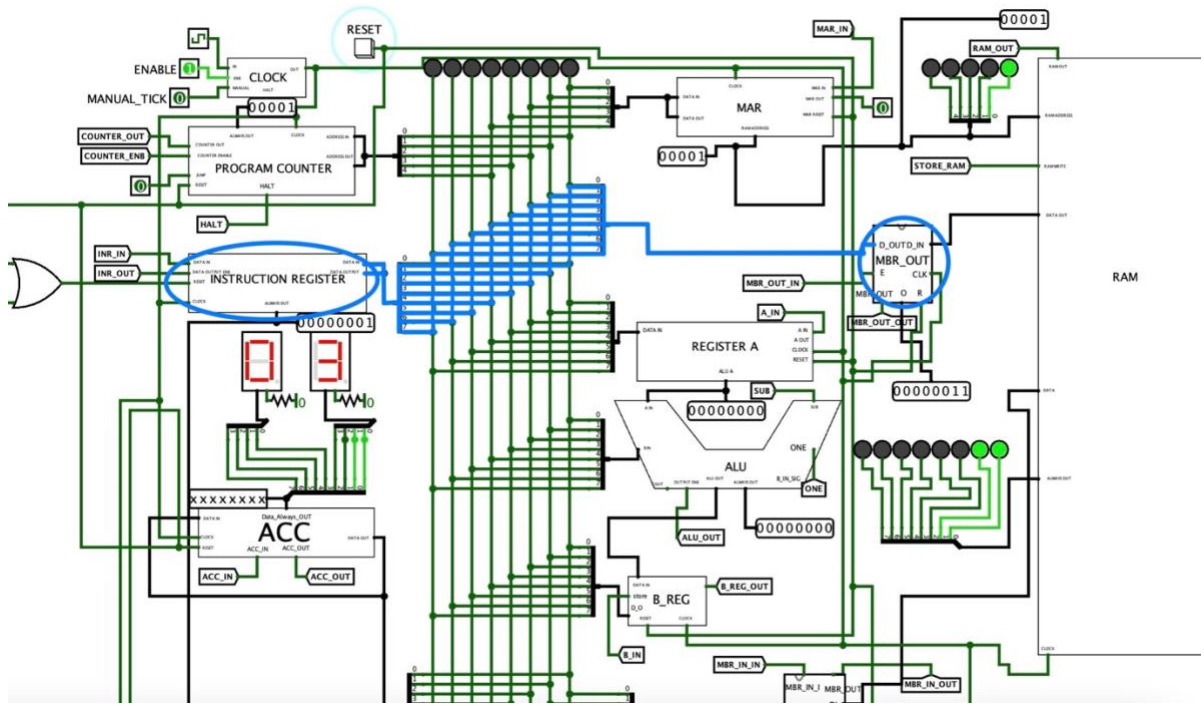
4. In the third CLOCK pulse, the MBR sends the content to the BUS, which enters the IR, and then the PC increments by one.



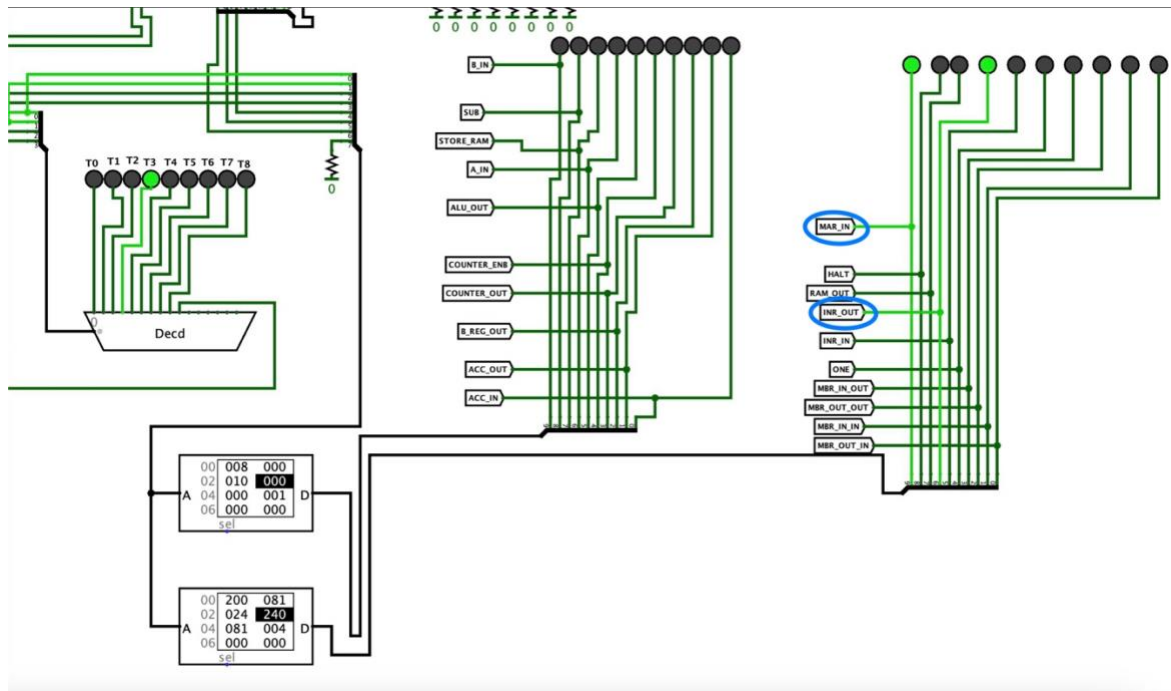5. The instruction is decoded by the CU.
6. The CU activates the INR\_OUT and MAR\_IN signals. (The 5 least significant bits end up in the MAR).



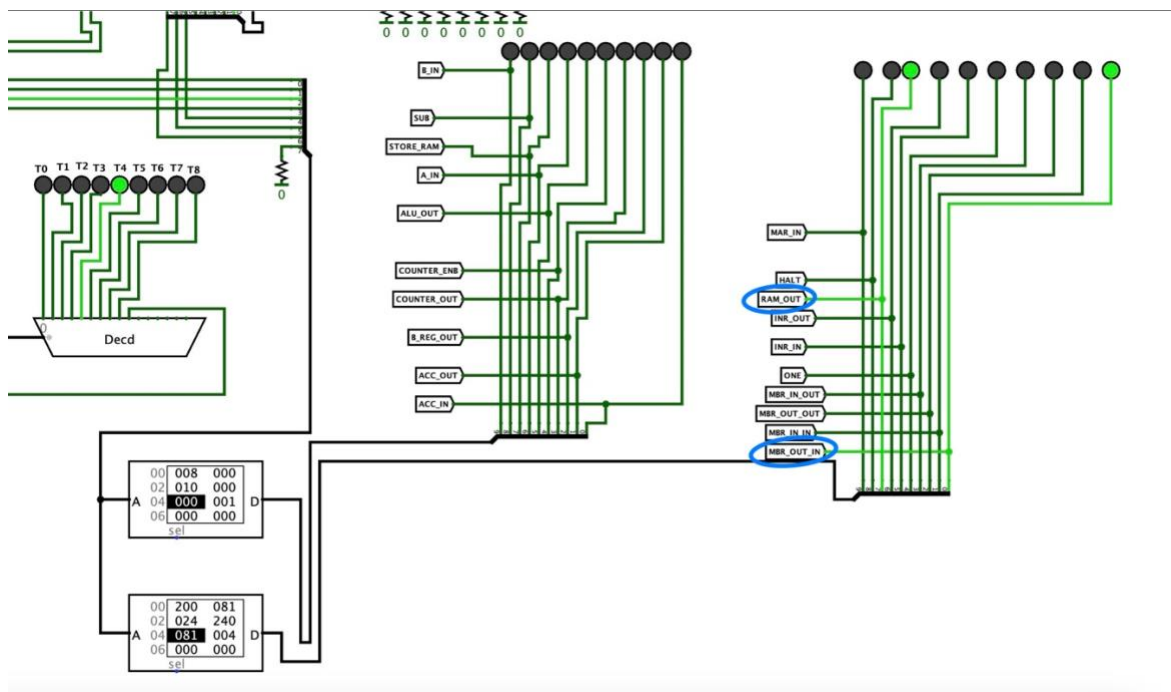- Then, the CU activates the RAM\_OUT and MBR\_IN signals. (The content that was inside the ADDRESS goes to the MBR).





8. Finally, the CU activates the MBR\_OUT signal and ACC\_IN. (The content that was in the register enters the ACC, loading the indicated value).

